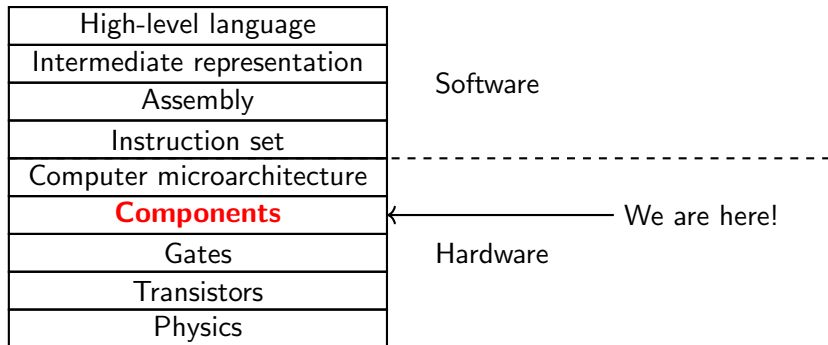


# Building with flip-flops and registers

## COMSM1302 Overview of Computer Architecture

John Lapinskas, University of Bristol

# From gates to components



Things are getting complex enough that we can't keep thinking of individual NAND gates any more!

We must abstract things into components/subcircuits — plexers, adders, registers, gates, and NANDs *only* when they are the right tool for the job.

These components will themselves become part of larger components...

## Registers as a building block: A counter

A **counter** stores and outputs a binary value *out* that goes up by 1 at (the rising edge of) each clock cycle. It has a single input: *reset*. If *reset* is 1 on a rising edge, the value in the counter is set back to 0.

How can we build a 16-bit counter from a 16-bit register?

## Registers as a building block: A counter

A **counter** stores and outputs a binary value  $out$  that goes up by 1 at (the rising edge of) each clock cycle. It has a single input:  $reset$ . If  $reset$  is 1 on a rising edge, the value in the counter is set back to 0.

How can we build a 16-bit counter from a 16-bit register?

Let's take the same approach as with the register and draw an informal "truth table" to express our next desired output  $out_{new}$  in terms of our inputs and the output  $out_{old}$  from the previous cycle.

$reset$	$out_{new}$
0	$out_{old} + 1$
1	0x0000

## Registers as a building block: A counter

A **counter** stores and outputs a binary value  $out$  that goes up by 1 at (the rising edge of) each clock cycle. It has a single input:  $reset$ . If  $reset$  is 1 on a rising edge, the value in the counter is set back to 0.

How can we build a 16-bit counter from a 16-bit register?


Let's take the same approach as with the register and draw an informal "truth table" to express our next desired output  $out_{new}$  in terms of our inputs and the output  $out_{old}$  from the previous cycle.

$reset$	$out_{new}$
0	$out_{old} + 1$
1	0x0000

We already know how to calculate  $out_{old} + 1$  from  $out_{old}$ : with an adder!

And as with the register, we can express this sort of "if zero then  $x$  otherwise  $y$ " logic neatly with a multiplexer.


# The counter in Logisim

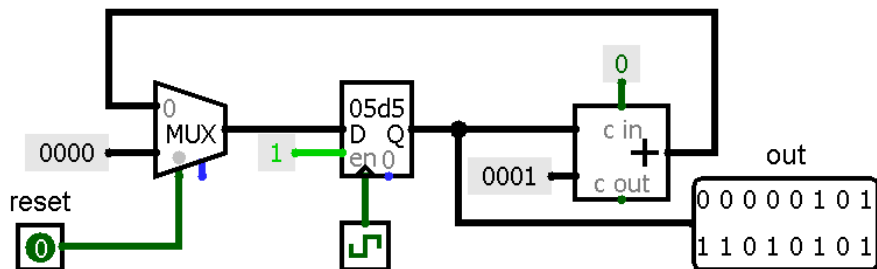

[See video for a demonstration and further explanation.  
The circuit is available for download from the unit page.]
 
## Flip-flops as a building block: A one-shot

A **one-shot** turns a 1 input into a pulse of 1 lasting for a single clock cycle:



This is useful for e.g. initialising registers at power-on, or turning long button-presses from a user into a more convenient form.

How can we build this out of flip-flops? It helps to break the circuit's behaviour down into **states** stored in flip-flops/registers.

# State diagrams

We want the one-shot to:

- a Wait for a 1 on *in*.
- b Send a pulse for one cycle.
- c Wait for a 0 on *in*, then go back to (a).

We can represent this as a diagram:




# State diagrams

We want the one-shot to:

- a Wait for a 1 on *in*.
- b Send a pulse for one cycle.
- c Wait for a 0 on *in*, then go back to (a).

We can represent this as a diagram:

 


# State diagrams

We want the one-shot to:

- a Wait for a 1 on *in*.
- b Send a pulse for one cycle.
- c Wait for a 0 on *in*, then go back to (a).

We can redraw this more compactly:

 


# State diagrams

We want the one-shot to:

- a Wait for a 1 on *in*.
- b Send a pulse for one cycle.
- c Wait for a 0 on *in*, then go back to (a).

We can redraw this more compactly:

 


# State diagrams

We want the one-shot to:

- a Wait for a 1 on *in*.
- b Send a pulse for one cycle.
- c Wait for a 0 on *in*, then go back to (a).

We can redraw this more compactly:

 

This is a **Moore machine**. It transitions between states each clock cycle based on its input, and its output is a function of its state.

We can store the state *S* as (e.g.) a binary number in a register/flip-flops. Then state transitions and outputs come from combinatorial logic!

## Building the one-shot

Say we store the state in two flip-flops  $XY$ , representing  $S0$ ,  $S1$  and  $S2$  as  $00$ ,  $01$  and  $10$  respectively. Then our truth tables are:

$X_{old}$	$Y_{old}$	$in$	$X_{new}$	$Y_{new}$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	0
1	1	X	X	X

We can take

$$X_{new} = (X_{old} \vee Y_{old}) \wedge in,$$

$$Y_{new} = \neg X_{old} \wedge \neg Y_{old} \wedge in.$$

# Building the one-shot

Say we store the state in two flip-flops  $XY$ , representing  $S0$ ,  $S1$  and  $S2$  as  $00$ ,  $01$  and  $10$  respectively. Then our truth tables are:

$X_{old}$	$Y_{old}$	$in$	$X_{new}$	$Y_{new}$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	0
1	1	X	X	X

$X$	$Y$	$out$
0	0	0
0	1	1
1	0	0
1	1	X


We can take  $out = Y$ .

We can take

$$X_{new} = (X_{old} \vee Y_{old}) \wedge in,$$

$$Y_{new} = \neg X_{old} \wedge \neg Y_{old} \wedge in.$$

## The one-shot in Logisim

 

[See video for a demonstration and further explanation.  
The circuit is available for download from the unit page.]

## A better one-shot: Mealy machines

Is this optimal? Definitely not! There are many tricks to do better, e.g. being very careful about encoding your state in the most useful way.

Here's one trick: By capturing the input in its own flip-flop/register, we can make the output depend on both the old state and the old input.

This means we can make the output depend on **transitions** between states, not just the state itself.




## A better one-shot: Mealy machines

Is this optimal? Definitely not! There are many tricks to do better, e.g. being very careful about encoding your state in the most useful way.

Here's one trick: By capturing the input in its own flip-flop/register, we can make the output depend on both the old state and the old input.

 This means we can make the output depend on **transitions** between states, not just the state itself.



Here e.g. “1/0” written near an arrow means that the transition between states happens on input 1, and results in output 0.

This is called a **Mealy machine**. Both Moore and Mealy machines are examples of **finite state machines**.

# Building a better one-shot

The truth table we need to make this Mealy machine is:

$S_{\text{old}}$	$in_{\text{old}}$	$S_{\text{new}}$	$out$
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0

$$S_{\text{new}} = in_{\text{old}},$$

$$out = \neg S_{\text{old}} \wedge in_{\text{old}}.$$


# Building a better one-shot

The truth table we need to make this Mealy machine is:

$S_{old}$	$in_{old}$	$S_{new}$	$out$
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0

$$S_{new} = in_{old},$$


$$out = \neg S_{old} \wedge in_{old}.$$

 

Much better! Notice we could also remove the NOT gate if we wanted, by using the  $Q'$  output of the state flip-flop instead of the  $Q$  output.
 
# General Moore and Mealy machines

You can implement **any** Moore/Mealy machine with the following schema:




The storage can be flip-flops or registers, but should be clocked.

The logic should be combinatorial (i.e. unclocked gates), and you can implement it by writing down the truth tables — like with the one-shot.
 
# General Moore and Mealy machines

You can implement **any** Moore/Mealy machine with the following schema:



Every Mealy machine

The storage can be flip-flops or registers, but should be clocked.

The logic should be combinatorial (i.e. unclocked gates), and you can implement it by writing down the truth tables — like with the one-shot.

# Less formal state diagrams

Suppose we want a vending machine to:

- a Wait for the user to enter the first digit of their snack.
- b Wait for the user to enter the second digit of their snack or hit “back” to erase the first digit.
- c Wait for the user to put in enough money to pay for their snack or hit “back” to cancel the transaction.
- d Dispense the snack (if the user didn’t hit “back”) and any change, then go back to (a).

This won’t be a “pure” Moore or Mealy machine — e.g. we’ll want to track the amount of money via a register. But we can and should still build the circuit by tracking an internal state.

# Less formal state diagrams

Suppose we want a vending machine to:

- a Wait for the user to enter the first digit of their snack.
- b Wait for the user to enter the second digit of their snack or hit “back” to erase the first digit.
- c Wait for the user to put in enough money to pay for their snack or hit “back” to cancel the transaction.
- d Dispense the snack (if the user didn’t hit “back”) and any change, then go back to (a).

This won’t be a “pure” Moore or Mealy machine — e.g. we’ll want to track the amount of money via a register. But we can and should still build the circuit by tracking an internal state.

Finite state machines are useful even in programming, as a way of simplifying complex control logic. For example, the platforming logic of Celeste is available [here](#), and is based around a finite state machine!